

1. Consider a circuit with an ideal 60 Hz generator with peak voltage of 120 V connected to a 2 H inductor and a  $2\Omega$  resistor connected in series. Find an expression for the current as a function of time.

2. Consider a LC circuit consisting of a ac generator, an inductor with inductance  $L$ , and a capacitor with capacitance  $C$  connected in series. What is the resonant frequency? If I swap out the inductor with an inductor with  $2x$  the inductance how does the resonant frequency change. What about if I swap out the capacitor with a capacitance  $2C$ ?

3. Consider an ac generator with frequency,  $f$ , with peak voltage  $V$ , connected in series with a resistor ( $R$ ), an inductor ( $L$ ) and a capacitor ( $C$ ). What is the current that flows through the capacitor? What is its rms voltage drop?

4. Same problem as above. What is its average power?